Device Information

ISL98602 Print Page

5 Channel DC/DC Converter + Von Slice + Power Good

- Features Description
- iSim Design Simulation
- Technical Documentation
 Pricing / Samples
- Tools And SupportRelated Devices

Datasheet



ISL98602

5 Channel DC/DC Converter + Von Slice + Power Good

Input Voltage (V)	9.5 to 15
V _{BOOST} (V)	10.83 to 19
Boost Current Limit (A)	5.5
V _{ON} (V)	up to 36
V _{OFF} (V)	down to -10
V _{LOGIC} (V)	(Vlogic1) 2.5 to 3.3 (Vlogic2) 0.9 to 2.0
# of V _{COM}	N/A
# of Gamma	N/A
Features	Automatic Start-Up Sequencing, fault protection
Input Voltage (min) (V)	9.5
Input Voltage (max) (V)	15
V _{BOOST} (min) (V)	10.83
V _{BOOST} (max) (V)	19
V _{ON} (min) (V)	*
V _{ON} (max) (V)	36
V _{OFF} (min) (V)	-10
V _{OFF} (max) (V)	*
V _{LOGIC} (min) (V)	2.5, 0.9
V _{LOGIC} (max) (V)	3.3, 2

Product Information

Key Features

9.5V to 15.0V Input Supply

1.3MHz Switching Frequency

5.5A Integrated Boost for Up to 19V A_{VDD}

V_{ON} Charge Pump, Up to 36V and 120mA

V_{OFF} Charge Pump, Down to -10V and 120mA

Synchronous Buck1 for 3.3V/2.5V with 2.0A Peak FET

Synchronous Buck2 Controller Output from 0.9V to 2.0V

On-board AVDD Delay Switch

V_{ON} Slice Function Integrated

Power Good Function for TCON Enable

Automatic Start-Up Sequencing

UVLO, UVP, OVP, OCP, and OTP Protection

40 Ld 6x6 QFN

Specified for Ambient Operation Over the -40°C to +85°C Temperature Range

Pb- Free (RoHS Compliant)

Description

The ISL98602 represents a high-power, integrated LCD supply IC targeted at large panel LCD displays. The ISL98602 integrates a high-power boost converter for AVDD generation, V_{ON} and V_{OFF} charge pump drivers, one synchronous buck regulator, and one synchronous buck controller for two logic voltages. The V_{ON} slicing circuitry and power good function are also included.

Operating at 1.3MHz, the AVDD boost converter features a 5.5A boost FET. Feedback is taken from the far side of the delay FET for improving regulation. The OVP circuit protects output side components.


The logic synchronous buck converter features two 2.3A FETs operating at 1.3MHz internal clock. The output voltage is set by the IC internally or with a feedback resistor. The soft-start circuitry is also integrated with the buck.

The second logic voltage is generated from a synchronous buck converter with MOSFET controllers. The overcurrent protection is also integrated with the buck.

The charge pump of V_{ON} and V_{OFF} uses the full switching frequency and integrates the driver for high current capability. V_{ON} is further processed through an integrated V_{ON} slice circuit in order to reduce flicker.

Alternative fixed voltages at the boost, Buck1, Buck2, V_{ON} charge pump, and V_{OFF} charge pump are available in ISL98602; please contact Intersil Marketing via e-mail at rmonteir@intersil.com.

Pricing / Packaging / Samples / Ordering

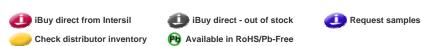

Part No.	Design-In Status	Temp.	Package	MSL	Price US \$	P	
ISL98602IRAAZ	Active	Ind	40 Ld QFN	3	2.50	V	-0
ISL98602IRAAZ-T	Active	Ind	40 Ld QFN T+R	3	2.50	V	
ISL98602IRAAZ-T7A	Active	Ind	40 Ld QFN T+R	3	2.75	V	
ISL98602IRAAZ-TK	Active	Ind	40 Ld QFN T+R	3	2.50	V	
ISL98602IRABZ	Active	Ind	40 Ld QFN	3	2.50	V	0
ISL98602IRABZ-T	Active	Ind	40 Ld QFN T+R	3	2.50	V	
ISL98602IRABZ-T7A	Active	Ind	40 Ld QFN T+R	3	2.75	V	
ISL98602IRABZ-TK	Active	Ind	40 Ld QFN T+R	3	2.50	•	

The price listed is the manufacturer's suggested retail price for quantities of 1K units. However, prices in today's market are fluid and may change without notice.

MSL = Moisture Sensitivity Level - per IPC/JEDEC J-STD-020

SMD = Standard Microcircuit Drawing

Technical Documentation

Datasheet(s):

5 Channel DC/DC Converter + V_{ON} Slice + Power Good

Technical Homepage: Display Products

Tools And Support

iSim Design Simulation

No Models Available

Application Block Diagrams

LCD-TV Panel

Applications

EL7515

LCD TV

Related Devices

High Frequency PWM Step-Up Regulator

EL7520 4-Channel DC/DC Controller

Parametric Table

EL7520A	4-Channel DC/DC Controller
EL7581	3-Channel DC/DC Converter
EL7583	3-Channel DC/DC Converter
EL7586	TFT-LCD Power Supply
EL7586A	TFT-LCD Power Supply
EL7640	TFT-LCD DC/DC with Integrated Amplifiers
EL7640A	TFT-LCD DC/DC with Integrated Amplifiers
EL7641	TFT-LCD DC/DC with Integrated Amplifiers
EL7641A	TFT-LCD DC/DC with Integrated Amplifiers
EL7642	TFT-LCD DC/DC with Integrated Amplifiers
EL7642A	TFT-LCD DC/DC with Integrated Amplifiers
ISL78010	Automotive Grade TFT-LCD Power Supply
ISL78020	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL78022	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL97516	600kHz/1.2MHz PWM Step-Up Regulator
ISL97519	1% Output Accuracy 600kHz/1.2MHz PWM Step-Up Regulator
ISL97519A	600kHz/1.2MHz PWM Step-Up Regulator
ISL97522	4-Channel TFT-LCD Supply
ISL97536	Monolithic 1A Step-Down Regulator with Low Quiescent Current
ISL97642	TFT-LCD DC/DC with Integrated Amplifiers
ISL97645	Boost + Von Slice + V _{COM}
ISL97645A	Boost + V _{ON} Slice + V _{COM} + Reset
ISL97646	Boost + LDO + V _{ON} Slice + V _{COM}
ISL97649A	TFT-LCD Supply + DCP + VCOM Amplifier + Gate Pulse Modulator + RESET
ISL97649B	TFT-LCD Supply + DCP + VCOM Amplifier + Gate Pulse Modulator + RESET
ISL97650	4-Channel Integrated LCD Supply
ISL97650B	4-Channel Integrated LCD Supply
ISL97651	4-Channel Integrated LCD Supply
ISL97652	4-Channel Integrated LCD Supply with Dual V _{COM} Amplifiers
ISL97653A	5-Channel Integrated LCD Supply
ISL97656	Integrated 4A Switch PWM Step-Up Regulator
ISL98012	1.8V Input PWM Step-Up Regulator

About Us | Careers | Contact Us | Investors | Legal | Privacy | Site Map | Subscribe | Intranet

5 Channel DC/DC Converter + V_{ON} Slice + Power-Good



©2003-2011. Intersil Americas Inc. All rights reserved.

ISL98603